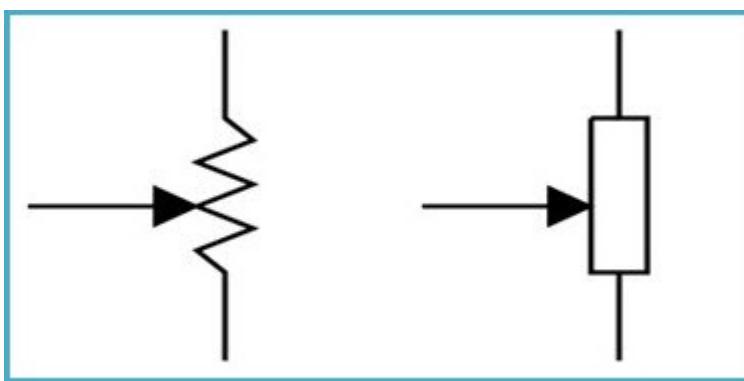


Potentiometer Construction, Working and Applications

The Potentiometer is an electric instrument that used to measure the [EMF \(electro motive force\)](#) of a given cell, the internal resistance of a cell. And also it is used to compare EMFs of different cells. It can also use as a [variable resistor](#) in most of the applications. These potentiometers are used in huge quantities in the manufacture of electronics equipment that provides a way of adjusting [electronic circuits](#) so that the correct outputs are obtained. Although their most obvious use must be for volume controls on radios and other electronic equipment used for audio.




Why is Potentiometer chosen over Voltmeter to measure the potential (EMF) of a cell? When we use Voltmeter, current flows through the circuit and because of the internal resistance of the cell, always terminal potential will be less than the actual cell potential. In this circuit, when the potential difference is balanced (using a Galvanometer null detection), no current flows in the circuit, so the terminal potential will be equal to the actual cell potential. So we can understand that the Voltmeter measures the terminal potential of a cell, but this measures actual cell potential. The schematic symbols of this is shown below.



Construction and Working Principle

The potentiometer consists of a long resistive wire L made up of magnum or with constantan and a battery of known EMF V . This voltage is called as **driver cell voltage**. Connect the two ends of the resistive wire L to the battery terminals as shown below; let us assume this is a primary circuit arrangement. One terminal of another cell (whose EMF E is to be measured) is at one end of the primary circuit and another end of the cell terminal is connected to any point on the resistive wire

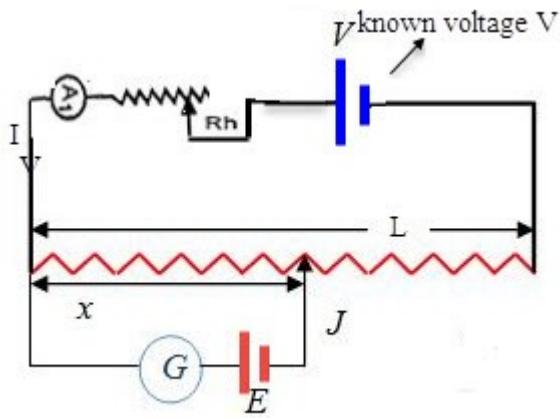through a galvanometer G. Now let us assume this arrangement is a secondary circuit. The arrangement of the potentiometer as shown below.



The basic working principle of this is based on the fact that the fall of the potential across any portion of the wire is directly proportional to the length of the wire, provided wire has uniform cross-sectional area and the constant current flowing through it. "When there is no potential difference between any two nodes there is electric current will flow".

Now the potentiometer wire is actually a wire with high resistivity (ρ) with uniform cross-sectional area A. Thus, throughout the wire, it has uniform resistance. Now this potentiometer terminal connected to the cell of high EMF V (neglecting its internal resistance) called driver cell or the voltage source. Let the current through the potentiometer is I and R is the total resistance of the potentiometer.

Then by Ohms law $V=IR$

We know that $R=\rho L/A$

Thus, $V= I \rho L/A$

As ρ and A are always constant and current I is kept constant by a rheostat.

So $L \rho/A=K$ (constant)

Thus, $V= KL$. Now suppose a cell E of lower EMF than the driver cell is put in the circuit as shown above. Say it has EMF E. Now in the potentiometer wire say at length x the potentiometer has become E.

$$E= L \rho x/A=Kx$$

When this cell be put in the circuit as shown above figure with a jokey connected to the corresponding length (x), there will be no flow of current through the galvanometer because when the potential difference is equal to zero, no current will flow through it. So the galvanometer G show null detection. Then the length (x) is called the length of the null point. Now by knowing the constant K and the length x. We can find the unknown EMF.

$$E= L \rho x/A=Kx$$


Secondly, EMF of two cells may also be compared, let the first cell of EMF E1 given a null point at a length= L1 and the second cell of EMF E2 show a null point at length= L2

Then,

Types of Potentiometers

A potentiometer is also commonly known as pot. These potentiometers have three terminal connections. One terminal connected to a sliding contact called wiper and the other two terminals are connected to a fixed resistance track. The wiper can be moved along the resistive track either by use of a linear sliding control or a rotary “wiper” contact. Both rotary and linear controls have the same basic operation.

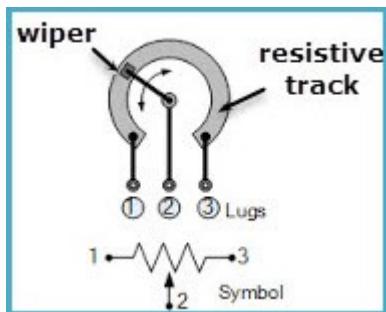The most common form of the potentiometer is the single turn rotary potentiometer. This type of potentiometer is often used in audio volume control (logarithmic taper) as well as many other applications. Different materials are used to construct potentiometers, including carbon composition, cermet, conductive plastic, and the metal film.



Rotary Potentiometers

These are the most common type of potentiometers, where the wiper moves along a circular path.

Type	Description	Applications
Single-turn pot	Single rotation of approximately 270 degrees or 3/4 of a full turn	Most common pot, used in applications where a single turn provides enough control resolution.
Multi-turn pot	Multiple rotations (mostly 5, 10 or 20), for increased precision. They are constructed either with a wiper that follows a spiral or helix form, or by using a worm-gear.	Used where high precision and resolution is required. The worm-gear multi turn pots are often used as trim pots on PCB.
Dual-gang pot	Two potentiometer combined on the same shaft, enabling the parallel setting of two channels. Most common are single turn potentiometers with equal resistance and taper. More than two gangs are possible but not very common.	Used in for example stereo audio volume control or other applications where 2 channels have to be adjusted in parallel.
Concentric pot	Dual potmeter, where the two potentiometers are individually adjusted by means of concentric shafts. Enables the use of two controls on one unit.	Often encountered in (older) car radios, where the volume and tone controls are combined.
Servo pot	A motorized potmeter which can also be automatically adjusted by a servo motor.	Used where manual and automatic adjustment is required. Often seen in audio equipment, where the remote-control can turn the volume control knob.

Linear



**Dual-gang
potentiometer**



**Concentric
potentiometer**



**Multi-turn
potentiometer**

Potentiometers

In these types of Potentiometers the wiper moves along a linear path. Also known as slide pot, slider, or fader.

Type	Description	Applications
Slide pot	Single linear slider potentiometer, for audio applications also known as a fader. High quality faders are often constructed from conductive plastic.	For single channel control or measurement of distance.
Dual-slide pot	Dual slide potentiometer, single slider controlling two potentiometers in parallel.	Often used for stereo control in professional audio or other applications where dual parallel channels are controlled.
Multi-turn slide	Constructed from a spindle which actuates a linear potentiometer wiper. Multiple rotations (mostly 5, 10 or 20), for increased precision.	Used where high precision and resolution is required. The multi turn linear pots are used as trim pots on PCB, but not as common as the worm-gear trimmer potentiometer.
Motorized fader	Fader which can be automatically adjusted by a servo motor.	Used where manual and automatic adjustment is required. Common in studio audio mixers, where the servo faders can be automatically moved to a saved configuration.



**Multi-turn linear
trimpot**




Slide potentiometer



Motorized fader

Applications of Potentiometers

Potentiometer as a Voltage Divider

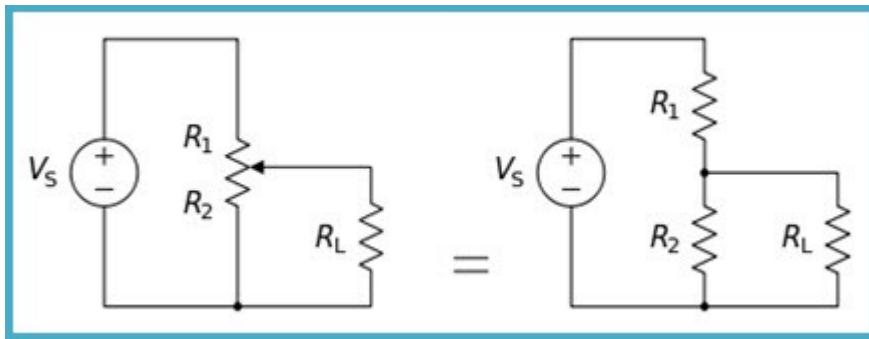


The potentiometer can be worked as [a voltage divider](#) to obtain a manual adjustable output voltage at the slider from a fixed input voltage applied across the two ends of the potentiometer. Now the load voltage across R_L can be measured as

$$V_L = R_2 R_L / (R_1 R_L + R_2 R_L + R_1 R_2)$$

Audio Control

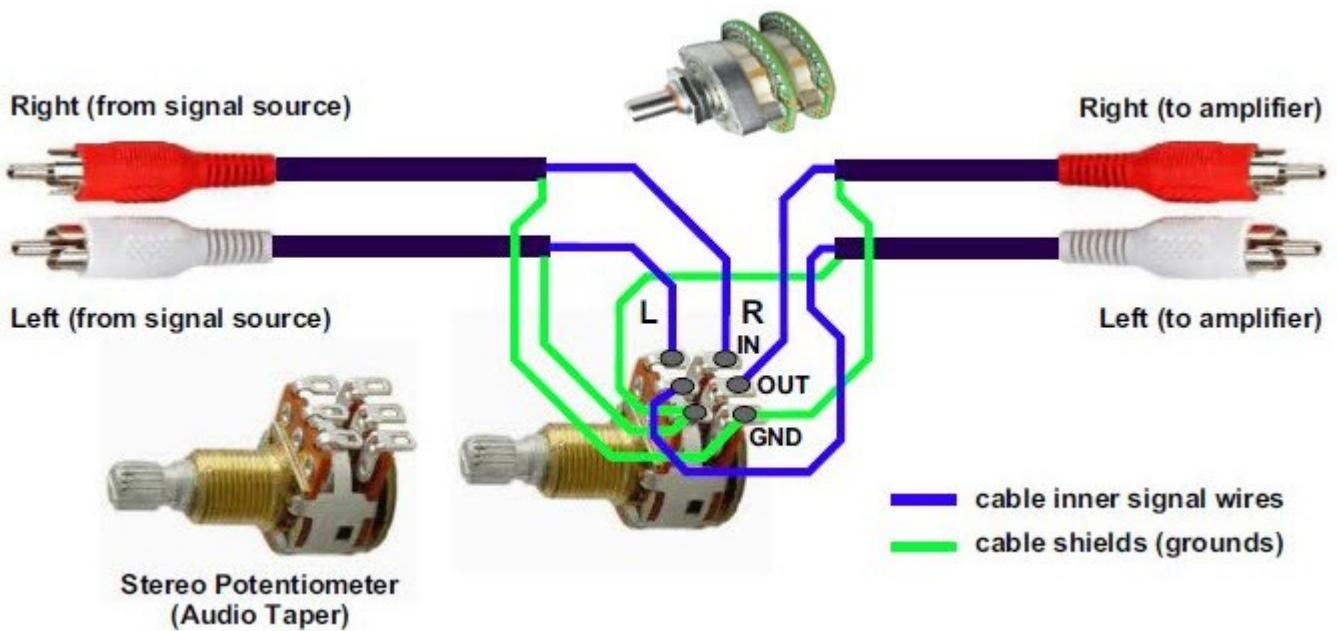Sliding potentiometers, one of the most common uses for modern low-power potentiometers are as audio control devices. Both sliding pots (faders) and rotary potentiometers (knobs) are regularly used to frequency attenuation, adjust loudness and for different characteristics of audio signals.




Television

Potentiometers were used to control the picture brightness, contrast, and colour response. A potentiometer was often used to adjust “vertical hold”, which affected the synchronization between the received picture signal and the receiver’s internal sweep circuit ([a multi-vibrator](#)).

Transducers

One of the most common application is measuring of displacement. To measure the displacement of the body, which is movable, is connected to the sliding element located on the potentiometer. As the

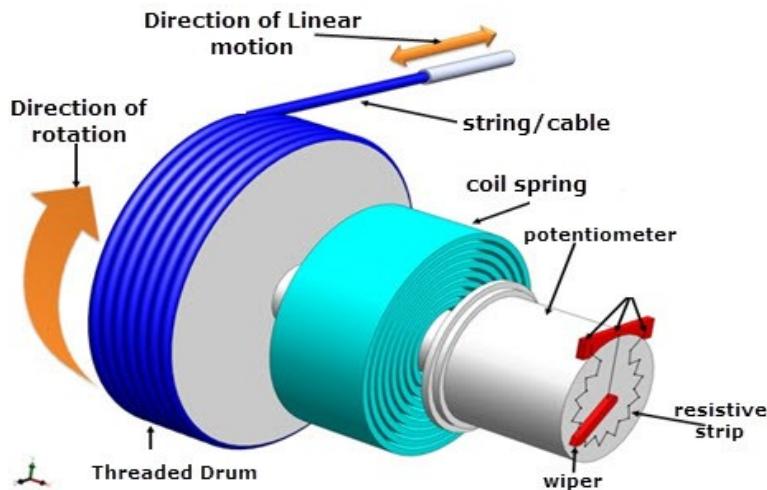body moves, the position of the slider also changes accordingly so the resistance between the fixed point and the slider changes. Due to this the voltage across these points also changes.



The change in resistance or the voltage is proportional to the change in the displacement of the body. Thus the voltage change indicates the displacement of the body. This can be used for the measurement of translational as well as rotational displacement. Since these potentiometers work on the principle of resistance, they are also called as the resistive potentiometers. For example, the shaft rotation might represent an angle, and the voltage division ratio can be made proportional to the cosine of the angle.