

UNIT-II NETWORK THEOREM

THEVENINS THEOREM:


In circuit theory, **Thévenin's theorem** for linear electrical networks states that any combination of voltage sources, current sources, and resistors with two terminals is electrically equivalent to a single voltage source V and a single series resistor R . For single frequency AC systems the theorem can also be applied to general impedances, not just resistors.

The procedure adopted when using Théveni determine the current in any branch of an active network (i.e. one containing a source of e.m.f.):

- (i) remove the resistance R from that branch,
- (ii) determine the open-circuit voltage, E , across the break,

remove each source of e.m.f. and replace them by their internal resistances and then determine the resistance, r , 'looking-in' break.

- (iv) determine the value of the current from the equivalent circuit shown in Figure 13.33, i.e. $I = \frac{E}{R+r}$

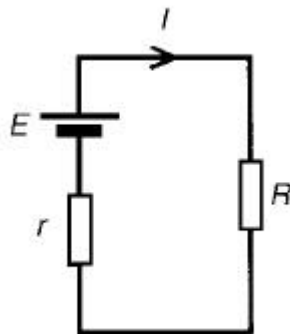


Problem 1: Use Thévenin's theorem to find the current flowing in the 10Ω resistor for the circuit shown in Figure


Following the above procedure:

The 10Ω resistance is removed from the circuit as shown in Figure There is no current flowing in the 5Ω resistor and current I_1 is given by:

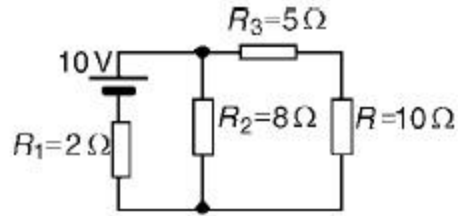
$$\begin{aligned} I_1 &= \frac{10}{R_1 + R_2} \\ &= \frac{10}{2 + 8} \\ &= 1\text{A} \end{aligned}$$




(a)

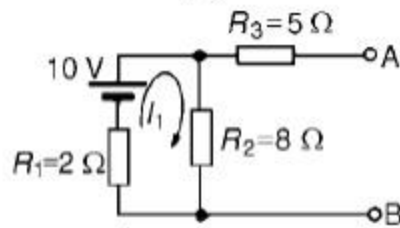

(b)

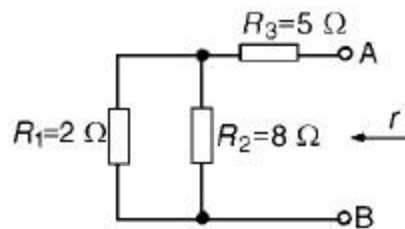

(c)

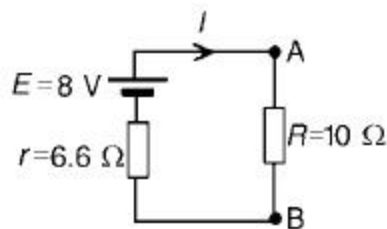

(d)

P.d. across $R_2 = I_1 R_2 = 1 \times 8 = 8\text{V}$ Hence p.d. across AB, i.e. the open-circuit voltage across the break, $E = 8\text{V}$

(iii) Removing the source of e.m.f. gives the circuit of Figure Resistance, $r = R_3 + R_1 R_2 / R_1 + R_2$

$$= 5 + (2 \times 8 / 2 + 8)$$

$$= 5 + 1.6 = 6.6 \Omega$$

(iv) The equivalent Thévenin's circuit is shown in F

Current $I = E/R+r = 8/10+6.6 = 8/16.6 = 0.482A$

Problem 2: For the network shown in Figure determine the current in the 0.8Ω resistor using Thévenin's theorem.

Following the procedure:


The 0.8Ω resistor is removed from the circuit as shown in Figure

Current $I_1 = 12/1+5+4 = 12/10$

$= 1.2A$

P.d. across 4Ω resistor $= 4I_1 = (4)(1.2) = 4.8V$

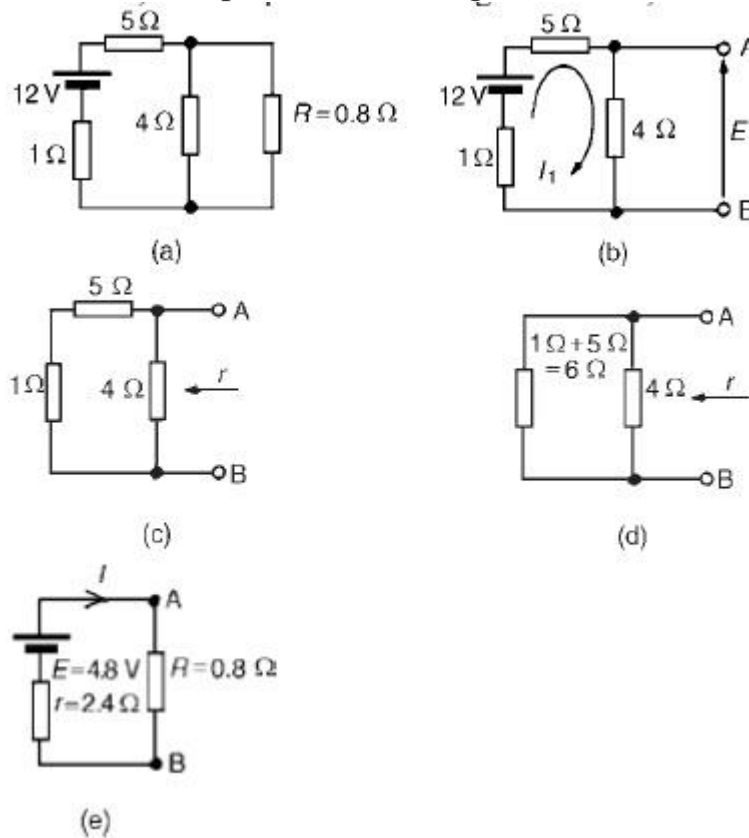Hence p.d. across AB, i.e. the open-circuit voltage across AB, $E = 4.8V$



(iii) Removing the source of e.m.f. gives the circuit shown in Figure (c). The equivalent circuit of Figure

(c) is shown in Figure (d), from which, resistance $r = 4 \times 6 / 4 + 6 = 24 / 10 = 2.4 \Omega$


(iv) The equivalent Thévenin's circuit $I = E / (R + r)$ is shown
 $= 4.8 / (2.4 + 0.8)$
 $= 4.8 / 3.2$

$I = 1.5\text{A}$ = current in the $0.8\ \Omega$ resistor

Problem 3: Use Thévenin's theorem to determine the current I flowing in the $4\ \Omega$ resistor shown in Figure.

Find also the power dissipated in the $4\ \Omega$ resistor.

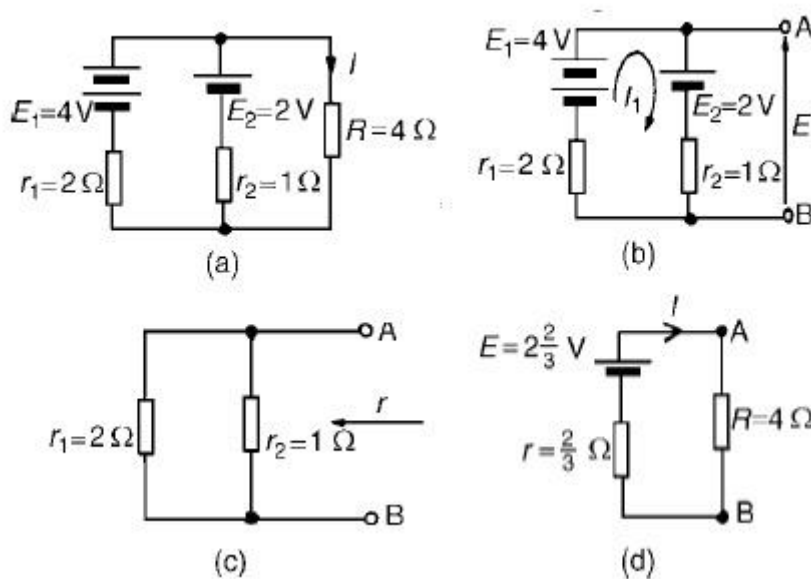(i) The $4\ \Omega$ resistor is removed from the circuit as shown in Figure



$$\begin{aligned} \text{(ii) Current } I &= E_1 - E_2/r_1 + r_2 \\ &= 4 - 2/2 + 1 \\ &= 2/3\text{A} \end{aligned}$$

$$\text{P.d. across AB, } E = E_1 - I_1 r_1 = 4 - \left(\frac{2}{3}\right)(2) = 2\frac{2}{3}\text{V}$$

(iii) Removing the sources of e.m.f. gives the circuit shown in Figure (c), from which resistance

$$r = 2 \times 1/2 + 1 = 2/3\ \Omega$$

(iv) The equivalent Thévenin's circuit is shown

$$\text{current, } I = \frac{E}{r + R} = \frac{2\frac{2}{3}}{\frac{2}{3} + 4} = \frac{8/3}{14/3}$$

$$= 8/14$$

$$= 0.571\text{A}$$

= current in the 4Ω resistor

Problem 4: Power dissipated in 4Ω resistor, $P = I^2 R = (0.571)^2 (4) = 1.304 \text{ W}$ Use Thévenin's t to determine the current flowing in the 3Ω resistance of the network shown in Figure (a). The

voltage source has negligible internal resistance.






i) The 3Ω resistance is removed from the circuit as shown in Figure (b).

(ii) The $1 \frac{2}{3} \Omega$ resistance now carries no current. P.d. across 10Ω resistor = $(10/10+5)(24)$

= **16V**

Hence p.d. across AB, $E = 16\text{V}$

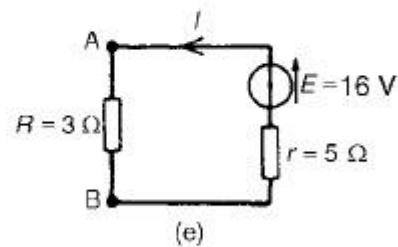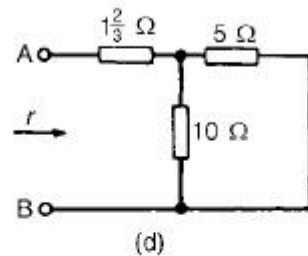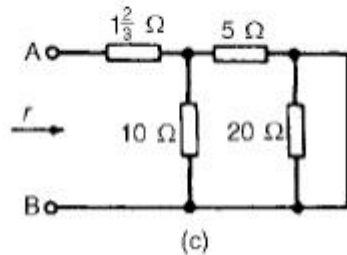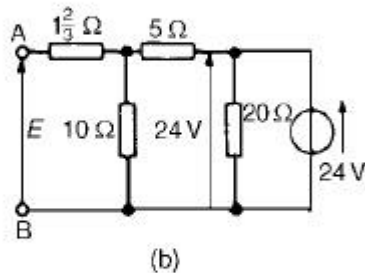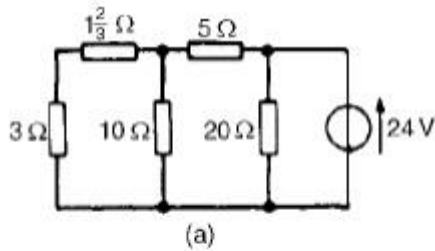(iii) Removing the source of e.m.f. and replacing it by its internal resistance means that the 20Ω resistance is short-circuited as shown in Figure (c) since its internal resistance is zero. The 20Ω resistance may thus be removed as shown in Figure (d)




From Figure (d), resistance,
 $r = 1 \frac{2}{3} + 10 \times 5 / 10 + 5 = 5 \Omega$


(iv) The equivalent Thévenin's circuit is shown current, $I = E/r + R = 16/3 + 5 = 16/8$

$$= 2A$$

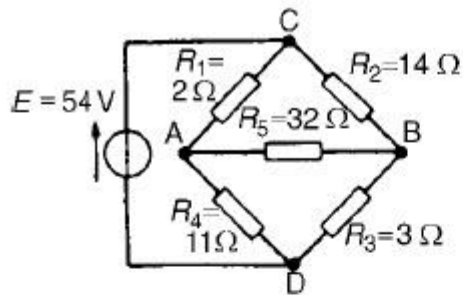
Problem 5: A Wheatstone Bridge network is shown in Figure (a). Calculate the current flowing in the 32Ω resistor, and its direction, using Thévenin negligible resistance.




(a)

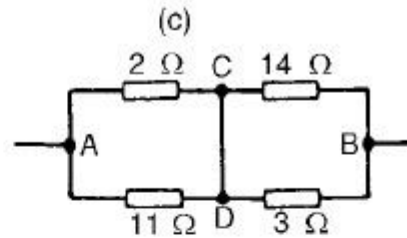


(d)

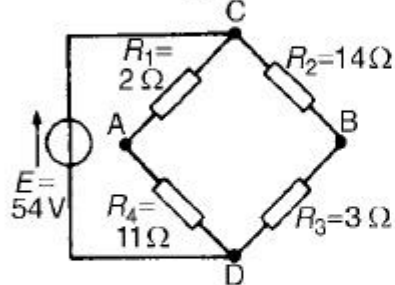


(b)

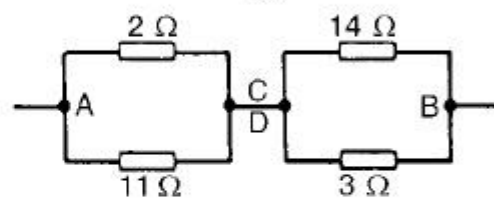

(e)

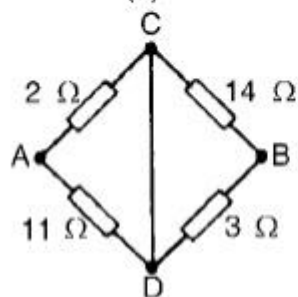

(c)

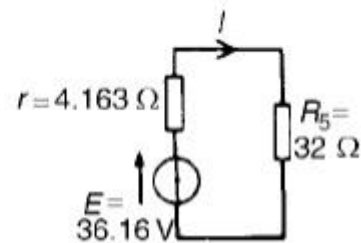

(f)

The 32Ω resistor is removed from the circuit as shown in Figure (b) The p.d. between A and C,

$$V_{AC} = R_1 / (R_1 + R_4) (E) = 2 / (2 + 11) (54) = 8.31V$$

The p.d. between B and C,

$V_{BC} = R_2/R_2 + R_3 (E) = 14/14 + 3(54) = 44.47V$ Hence the p.d. between A and B = $44.47 - 8.31 = 36.16V$

Point C is at a potential of +54V. Between C and A is a voltage drop of 8.31V. Hence the voltage at point A is $54 - 8.31 = 45.69V$. Between C and B is a voltage drop of 44.47V. Hence the voltage at point B is $54 - 44.47 = 9.53V$. Since the voltage at A is greater than at B, current must flow in the direction A to B.

Replacing the source of e.m.f. with a short-circuit (i.e. zero internal resistance) gives the circuit shown in Figure (c). The circuit is redrawn and simplified as shown in Figure (d) and (e), from which the resistance between terminals A and B,

$$\begin{aligned} r &= 2 \times 11/2 + 11 + 14 \times 3/14 + 3 \\ &= 22/13 + 42/17 \\ &= 1.692 + 2.471 = 4.163 \Omega \end{aligned}$$

(iv) The equivalent Thévenin's circuit is shown
current $I = E/r + R_5$

$$= 36.16/4.163 + 32 = 1A$$

NORTON'S THEOREM:

Norton's theorem states the following:

Any two-terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a current and a parallel resistor.

The steps leading to the proper values of I_N and R_N . Preliminary steps:

1. Remove that portion of the network across which the Norton equivalent circuit is found.
2. Mark the terminals of the remaining two-terminal network.
3. Finding R_N :

Calculate R_N by first setting all sources to zero and then finding the resultant resistance between the two marked terminals. Since $R_N = R_{Th}$ the procedure and value obtained using the approach described for Thevenin's theorem will determine the proper value of R_N .

4. Finding I_N :

Calculate I_N by first returning all the sources to their original position and then finding the short-circuit current between the marked terminals. It is the same current that would be measured by an ammeter placed between the marked terminals.

5. Draw the Norton equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.

Problem 1: Use Norton's theorem to determine Ω resistance for the the cur circuit shown in Figure

The branch containing the 10Ω resistance is short circuited as shown in Figure Figure (c) is equivalent to Figure (b).Hence $I_{SC} = 10/2$

$$= 5A$$


If the $10V$ source of e.m.f. is removed from Figure (b) the resistance 'looking-in' at a break made between A and B is given by:

$$r = 2 \times 8/2 + 8 = 1.6 \Omega$$


From the Norton equivalent network shown in Figure(d) the current in the 10Ω resistance, by current division, is given by:

$$I = (1.6/1.6 + 5 + 10) (5) = 0.482A$$

as obtained previously in problem 7 using Thévenin's theorem.

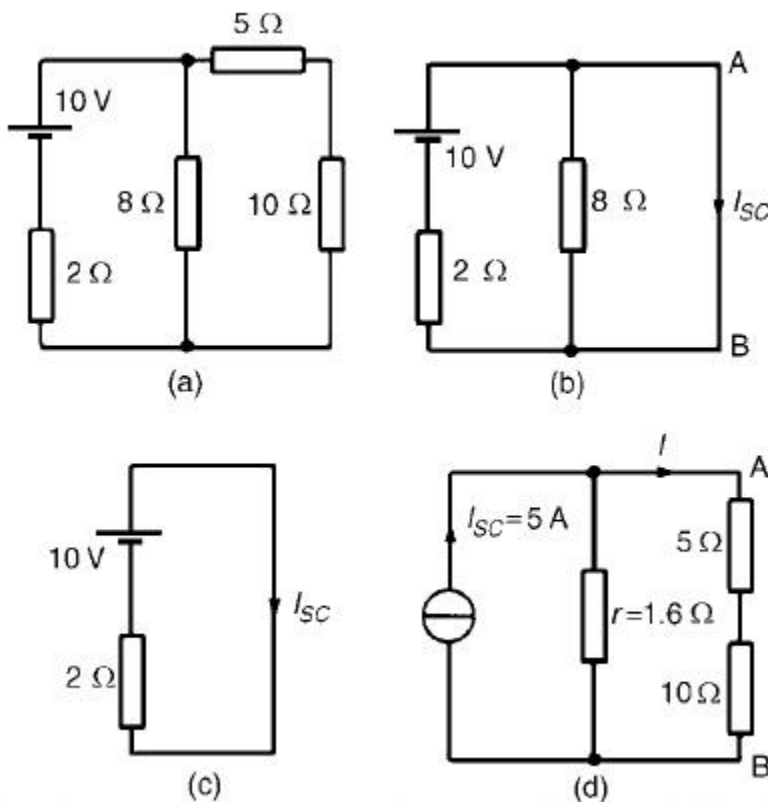

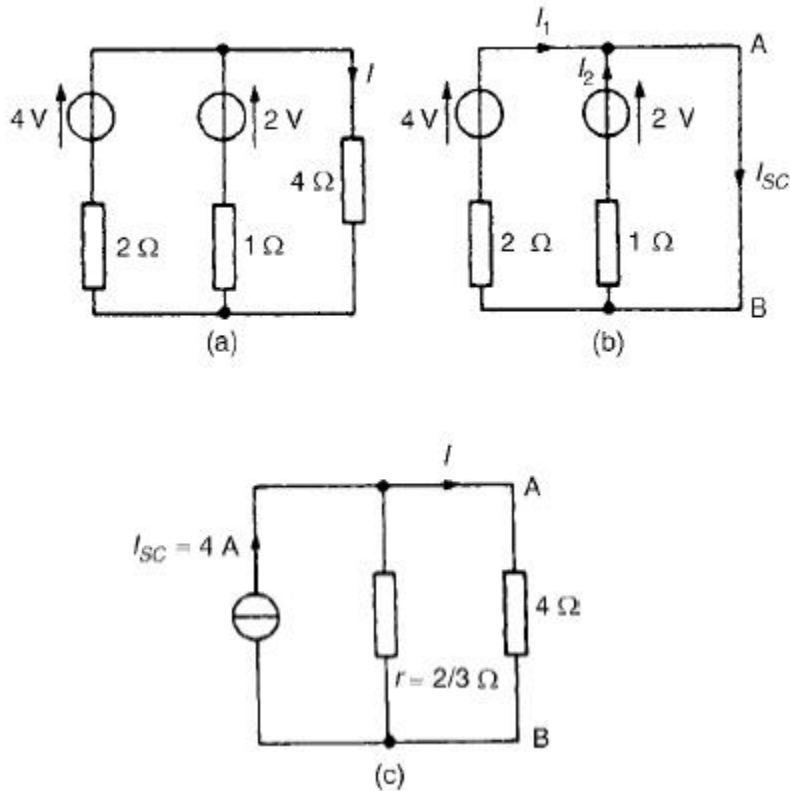Problem 2: Use Norton's theorem to determine the current I flowing in the $4\ \Omega$ resistance shown in Figure (a).



The $4\ \Omega$ branch is short-circuited as shown in Figure (b). From Figure (b), $I_{sc} = I_1 + I_2 = 4\ \text{A}$

If the sources of e.m.f. are removed the resistance 'looking-in' at a break made be given by:

$$r = 2 \times \frac{1}{2} + 1 = \frac{2}{3}\ \Omega$$

From the Norton equivalent network shown in Figure (c) the current in the $4\ \Omega$ resistance is given by:

$$I = \left(\frac{2/3}{2/3 + 4} \right) (4) = 0.571\ \text{A},$$

Superposition theorem

Superposition theorem is based on the concept of linearity between the response and excitation of an electrical circuit. It states that the response in a particular branch of a linear circuit when multiple independent sources are acting at the same time is equivalent to the sum of the responses due to each independent source acting at a time.

In this method, we will consider only **one independent source** at a time. So, we have to eliminate the remaining independent sources from the circuit. We can eliminate the voltage sources by shorting their two terminals and similarly, the current sources by opening their two terminals.

Therefore, we need to find the response in a particular branch '**n**' **times** if there are '**n**' independent sources. The response in a particular branch could be either current flowing through that branch or voltage across that branch.

Procedure of Superposition Theorem

Follow these steps in order to find the response in a particular branch using superposition theorem.


Step 1 – Find the response in a particular branch by considering one independent source and eliminating the remaining independent sources present in the network.

Step 2 – Repeat Step 1 for all independent sources present in the network.


Step 3 – Add all the responses in order to get the overall response in a particular branch when all independent sources are present in the network.

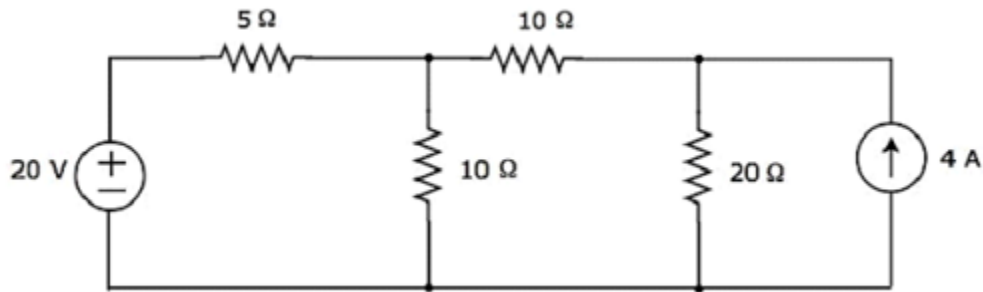Example


Find the current flowing through 20 Ω resistor of the following circuit using **superposition theorem**.



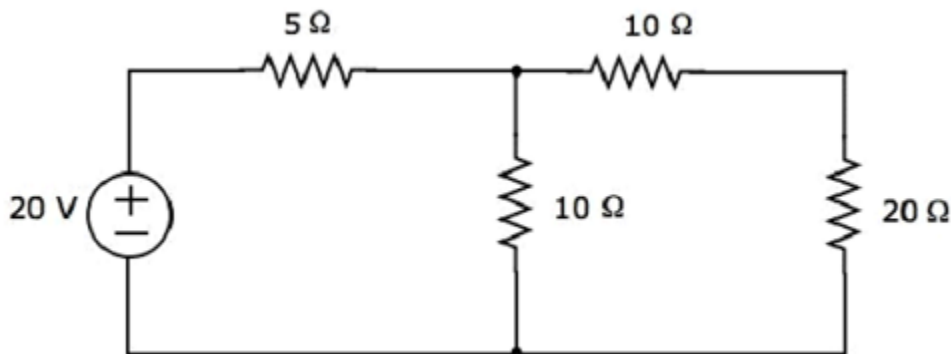Step 1 – Let us find the current flowing through $20\ \Omega$ resistor by considering only **20 V voltage source**. In this case, we can eliminate the 4 A current source by making open circuit of it. The modified circuit diagram is shown in the following figure.



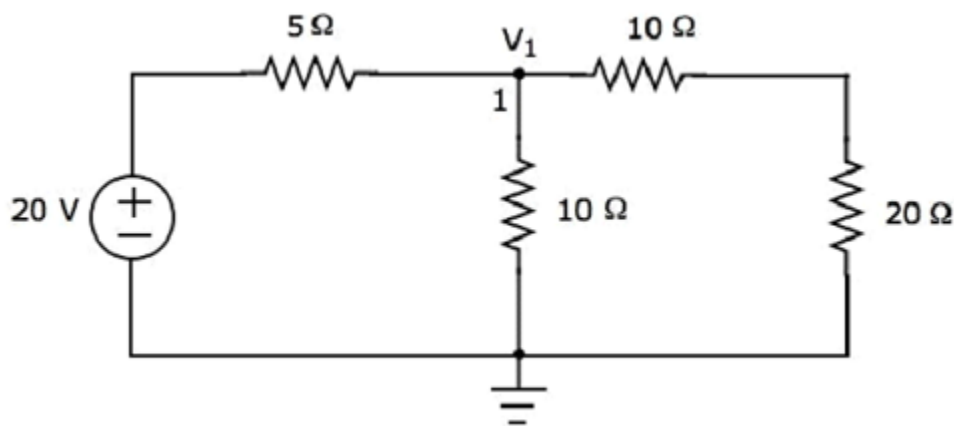There is only one principal node except Ground in the above circuit. So, we can use **nodal analysis** method. The node voltage V_1 is labelled in the following figure. Here, V_1 is the voltage from node 1 with respect to ground.



The **nodal equation** at node 1 is

$$V_1 - 205 + V_{110} + V_{110} + 20 = 0 \quad V_1 - 205 + V_{110} + V_{110} + 20 = 0$$

$$\Rightarrow 6V_1 - 120 + 3V_1 + V_{130} = 0 \Rightarrow 6V_1 - 120 + 3V_1 + V_{130} = 0$$

$$\Rightarrow 10V_1 = 120 \Rightarrow 10V_1 = 120$$

$$\Rightarrow V_1 = 12V \Rightarrow V_1 = 12V$$

The **current flowing through 20 Ω resistor** can be found by doing the following simplification.


$$I_1 = V_{110} + 20 \quad I_1 = V_{110} + 20$$

Substitute the value of V_1 in the above equation.

$$I_1 = 12/10 + 20 = 12/30 = 0.4A \quad I_1 = 12/10 + 20 = 12/30 = 0.4A$$

Therefore, the current flowing through 20 Ω resistor is **0.4 A**, when only 20 V voltage source is considered.

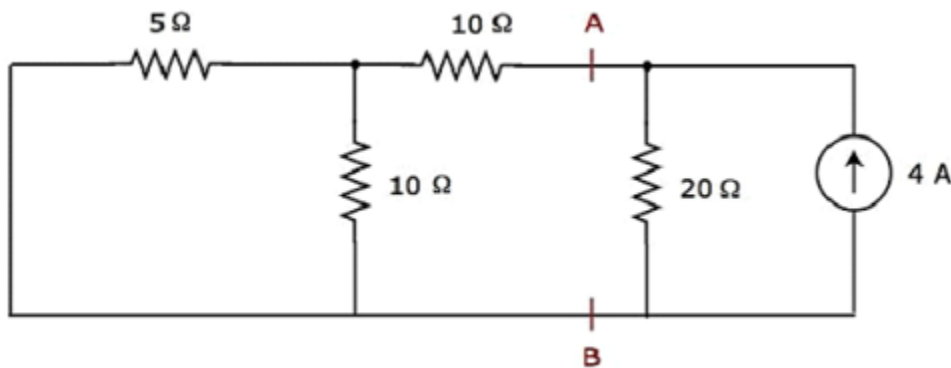Step 2 – Let us find the current flowing through 20 Ω resistor by considering only **4 A current source**. In this case, we can eliminate the 20 V voltage source by making short-circuit of it. The modified circuit diagram is shown in the following figure.




In the above circuit, there are three resistors to the left of terminals A & B. We can replace these resistors with a single **equivalent resistor**. Here, 5 Ω & 10 Ω resistors are connected in parallel and the entire combination is in series with 10 Ω resistor.

The **equivalent resistance** to the left of terminals A & B will be

$$R_{AB} = \left[\frac{5 \times 10}{5 + 10} + 10 \right] + 10 = 10.3 + 10 = 20.3 \Omega \quad R_{AB} = \left[\frac{5 \times 10}{5 + 10} + 10 \right] + 10 = 10.3 + 10 = 20.3 \Omega$$

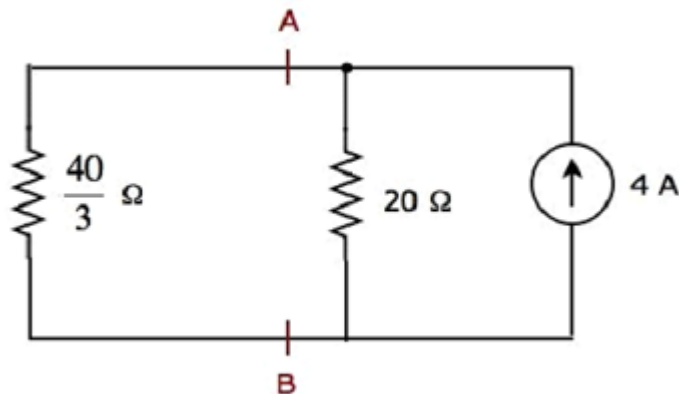The simplified circuit diagram is shown in the following figure.



We can find the current flowing through $20\ \Omega$ resistor, by using **current division principle**.

$$I_2 = I_S \left(\frac{R_1}{R_1 + R_2} \right) \quad I_2 = I_S \left(\frac{R_1}{R_1 + R_2} \right)$$

Substitute $I_S = 4\text{ A}$, $R_1 = 40/3\ \Omega$ and $R_2 = 20\ \Omega$ in the above equation.

$$I_2 = 4 \left(\frac{40/3}{40/3 + 20} \right) = 4 \left(\frac{40}{40 + 60} \right) = 1.6\text{ A} \quad I_2 = 4 \left(\frac{40/3}{40/3 + 20} \right) = 4 \left(\frac{40}{100} \right) = 1.6\text{ A}$$

Therefore, the current flowing through $20\ \Omega$ resistor is **1.6 A**, when only 4 A current source is considered.

Step 3 – We will get the current flowing through $20\ \Omega$ resistor of the given circuit by doing the **addition of two currents** that we got in step 1 and step 2. Mathematically, it can be written as

$$I = I_1 + I_2 = I_1 + I_2$$

Substitute, the values of I_1 and I_2 in the above equation.

$$I = 0.4 + 1.6 = 2\text{ A} \quad I = 0.4 + 1.6 = 2\text{ A}$$

Therefore, the current flowing through $20\ \Omega$ resistor of given circuit is **2 A**.

Maximum power transfer theorem

Maximum power transfer theorem states that the DC voltage source will deliver maximum power to the variable load resistor only when the load resistance is equal to the source resistance.


Similarly, **Maximum power transfer theorem** states that the AC voltage source will deliver maximum power to the variable complex load only when the load impedance is equal to the complex conjugate of source impedance.

In this chapter, let us discuss about the maximum power transfer theorem for DC circuits.

Proof of Maximum Power Transfer Theorem

Replace any two terminal linear network or circuit to the left side of variable load resistor having resistance of R_L ohms with a Thevenin's equivalent circuit. We know that Thevenin's equivalent circuit resembles a practical voltage source.

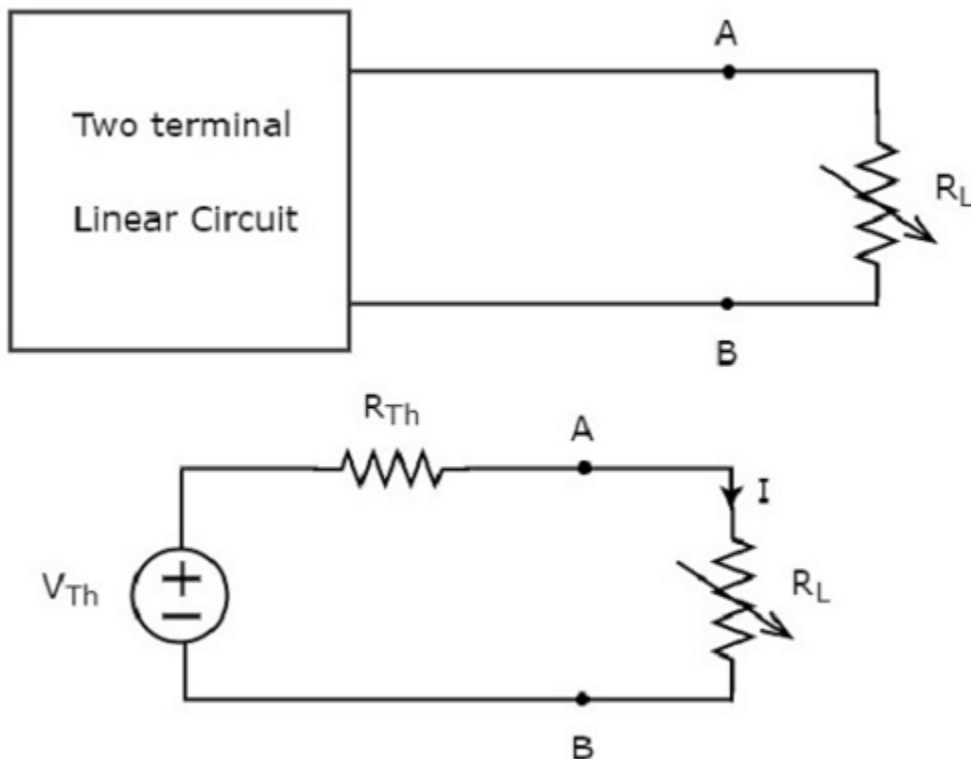This concept is illustrated in following figures.



The amount of power dissipated across the load resistor is

$$P_L = I^2 R_L \quad P_L = I^2 R_L$$

Substitute $I = \frac{V_{Th}}{R_{Th} + R_L} = \frac{V_{Th}}{R_{Th} + R_L}$ in the above equation.

$$P_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L \quad P_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

$$\Rightarrow P_L = \frac{V_{Th}^2 \{ R_L (R_{Th} + R_L) \}}{(R_{Th} + R_L)^2} \Rightarrow P_L = \frac{V_{Th}^2 \{ R_L (R_{Th} + R_L) \}}{(R_{Th} + R_L)^2} \quad \text{Equation 1}$$

Condition for Maximum Power Transfer

For maximum or minimum, first derivative will be zero. So, differentiate Equation 1 with respect to R_L and make it equal to zero.

$$\frac{dP_L}{dR_L} = \frac{V_{Th}^2 \{ (R_{Th} + R_L)^{-2} \times 1 - R_L \times 2(R_{Th} + R_L)^{-3} \}}{(R_{Th} + R_L)^4} = 0 \quad \frac{dP_L}{dR_L} = \frac{V_{Th}^2 \{ (R_{Th} + R_L)^{-2} \times 1 - R_L \times 2(R_{Th} + R_L)^{-3} \}}{(R_{Th} + R_L)^4} = 0$$

$$\Rightarrow (R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L) = 0 \Rightarrow (R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L) = 0$$

$$\Rightarrow (R_{Th} + R_L)(R_{Th} + R_L - 2R_L) = 0 \Rightarrow (R_{Th} + R_L)(R_{Th} + R_L - 2R_L) = 0$$

$$\Rightarrow (R_{Th} - R_L) = 0 \Rightarrow (R_{Th} - R_L) = 0$$

$$\Rightarrow R_{Th} = R_L \text{ or } R_L = R_{Th} \Rightarrow R_{Th} = R_L \text{ or } R_L = R_{Th}$$

Therefore, the **condition for maximum power** dissipation across the load is $R_L = R_{Th}$. That means, if the value of load resistance is equal to the value of source resistance i.e., Thevenin's resistance, then the power dissipated across the load will be of maximum value.

The value of Maximum Power Transfer

Substitute $R_L = R_{Th}$ & $P_L = P_{L,Max}$ in Equation 1.

$$P_{L,Max} = \frac{V_{Th}^2 \{ R_{Th} (R_{Th} + R_{Th}) \}}{(R_{Th} + R_{Th})^2} \quad P_{L,Max} = \frac{V_{Th}^2 \{ R_{Th} (R_{Th} + R_{Th}) \}}{(R_{Th} + R_{Th})^2}$$

$$P_{L,Max} = \frac{V_{Th}^2 \{ R_{Th}^4 R_{Th}^2 \}}{(R_{Th}^4 R_{Th}^2)} \quad P_{L,Max} = \frac{V_{Th}^2 \{ R_{Th}^4 R_{Th}^2 \}}{(R_{Th}^4 R_{Th}^2)}$$

$$\Rightarrow P_{L,Max} = \frac{V_{Th}^2}{4R_{Th}} \Rightarrow P_{L,Max} = \frac{V_{Th}^2}{4R_{Th}}$$

$$\Rightarrow P_{L,Max} = \frac{V_{Th}^2}{4R_L}, \text{ since } R_L = R_{Th} \Rightarrow P_{L,Max} = \frac{V_{Th}^2}{4R_L}, \text{ since } R_L = R_{Th}$$

Therefore, the **maximum amount of power** transferred to the load is

$$P_{L,Max} = V_{Th}^2 / 4R_L = V_{Th}^2 / 4R_{Th}$$

Efficiency of Maximum Power Transfer

We can calculate the efficiency of maximum power transfer, η_{Max} using following formula.

$$\eta_{Max} = \frac{P_{L,Max}}{P_S} \quad \text{Equation 2}$$

Where,

- $P_{L,Max}$ is the maximum amount of power transferred to the load.
- P_S is the amount of power generated by the source.

The **amount of power generated** by the source is

$$P_S = I^2 R_{Th} + I^2 R_L$$

$$\Rightarrow P_S = 2I^2 R_{Th}, \text{ since } R_L = R_{Th}$$

- Substitute $I = \frac{V_{Th}}{2R_{Th}}$ in the above equation.

$$P_S = 2 \left(\frac{V_{Th}}{2R_{Th}} \right)^2 R_{Th}$$

$$\Rightarrow P_S = 2 \left(\frac{V_{Th}^2}{4R_{Th}^2} \right) R_{Th}$$

$$\Rightarrow P_S = \frac{V_{Th}^2}{2R_{Th}}$$

- Substitute the values of $P_{L,Max}$ and P_S in Equation 2.

$$\eta_{Max} = \frac{V_{Th}^2 / 4R_{Th}}{V_{Th}^2 / 2R_{Th}}$$

$$\Rightarrow \eta_{Max} = \frac{1}{2} \Rightarrow \eta_{Max} = 50\%$$

We can represent the efficiency of maximum power transfer in terms of **percentage** as follows –

$$\% \eta_{Max} = \eta_{Max} \times 100\%$$


$$\Rightarrow \% \eta_{Max} = \left(\frac{1}{2} \right) \times 100\%$$

$$\Rightarrow \% \eta_{Max} = 50\%$$


Therefore, the efficiency of maximum power transfer is **50 %**.

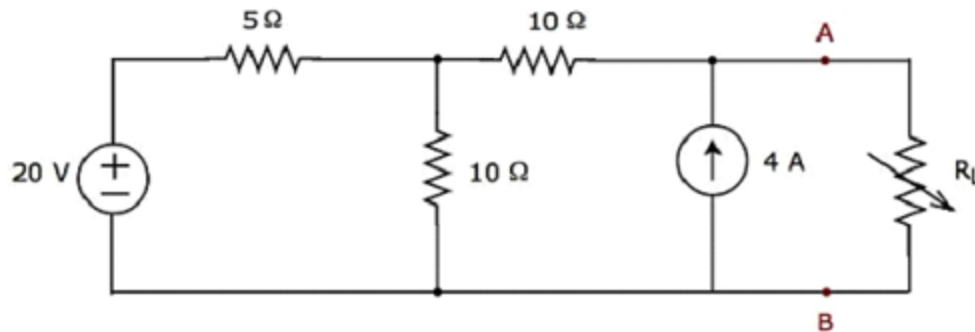Example

Find the **maximum power** that can be delivered to the load resistor R_L of the circuit shown in the following figure.




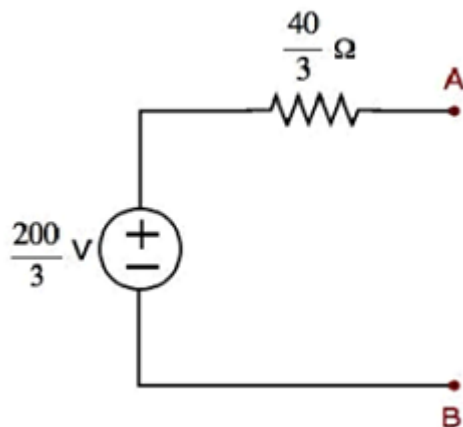Step 1 – In Thevenin's Theorem chapter, we calculated the Thevenin's equivalent circuit to the left side of terminals A & B. We can use this circuit now. It is shown in the following figure.



Here, Thevenin's voltage $V_{Th} = 200/3 \text{ V}$ and Thevenin's resistance $R_{Th} = 40/3 \Omega$

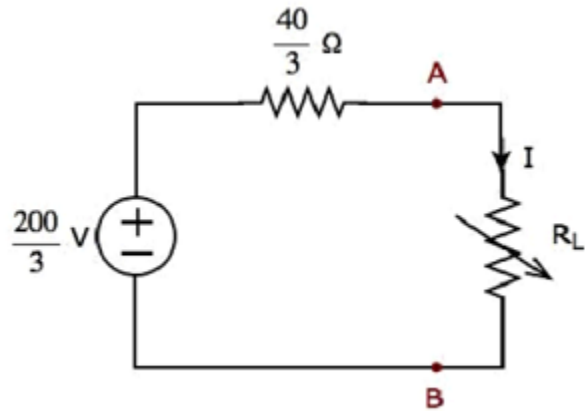Step 2 – Replace the part of the circuit, which is left side of terminals A & B of the given circuit with the above Thevenin's equivalent circuit. The resultant circuit diagram is shown in the following figure.



Step 3 – We can find the maximum power that will be delivered to the load resistor, R_L by using the following formula.

$$P_{L,Max} = \frac{V_{Th}^2}{4R_{Th}}$$

Substitute $V_{Th} = 200/3 \text{ V}$ and $R_{Th} = 40/3 \Omega$ in the above formula.

$$P_{L,Max} = \frac{(200/3)^2}{4(40/3)}$$

$$P_{L,Max} = 2503 \text{ W}$$

Therefore, the **maximum power** that will be delivered to the load resistor R_L of the given circuit is **2503 W**